
Nama : Cecylia Ivanka Hermanita


NIM : L200180210


Kelas : G

### Tugas Modul 4

#### Nomor 1

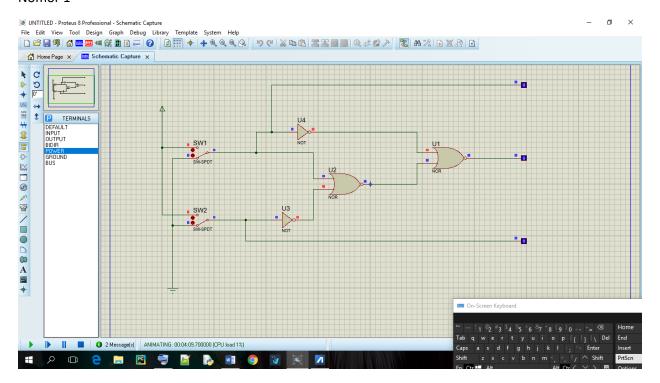

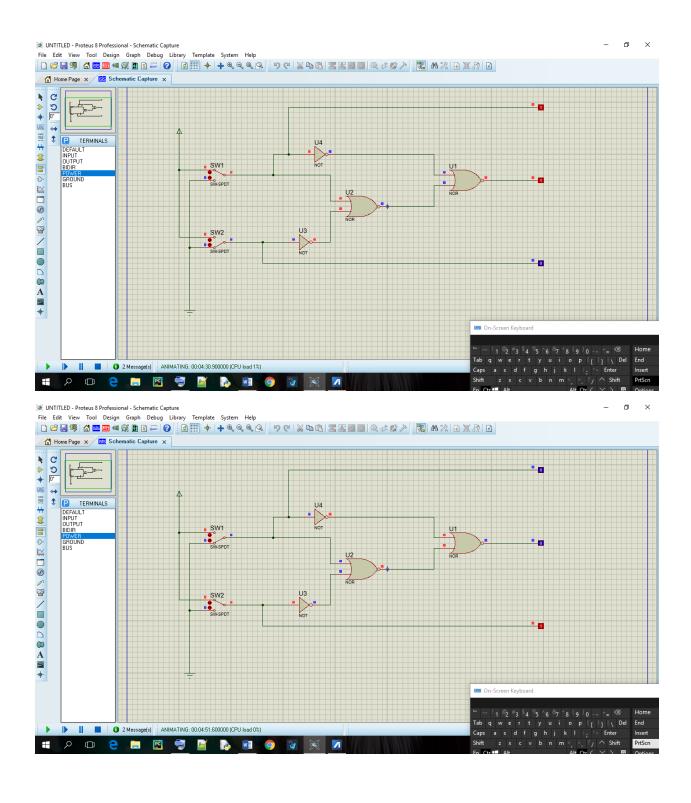


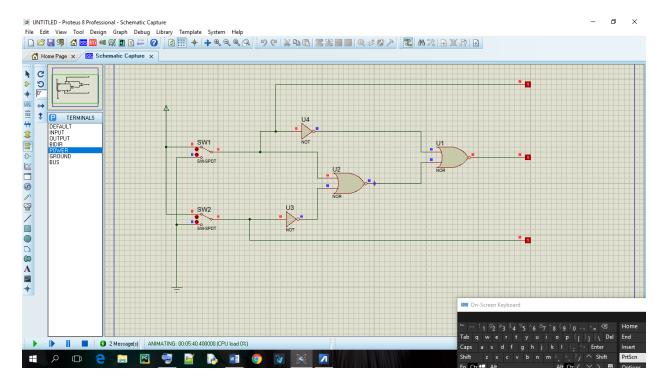

### Tabel Kebenaran

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1


# Diagram Waktu

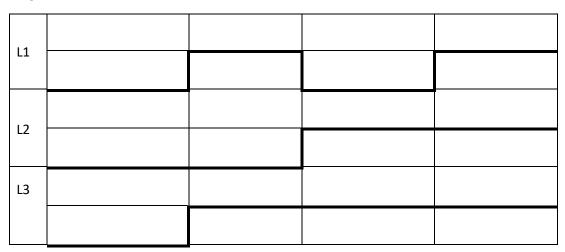

Fungsi Boolean

L3=L1+(L1+L2)

### Nomor 2

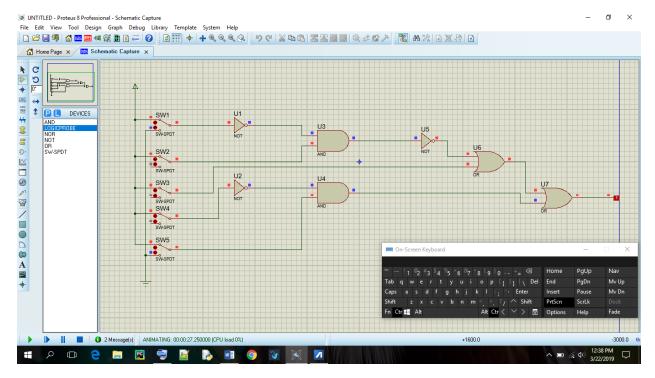

## CFungsi Boolean

$$F = (\overline{A \cdot B} + C) + (\overline{D} \cdot E)$$